R.C.M. & E.


DESIGN BOOKLET TWO

GALLATROL

COMPLETE GALLOPING GHOST PROPORTIONAL CONTROL SYSTEM

Assembly instructions for Tx, Rx, and Servo All Transistor, Relayless and with P.C. construction

Designed by T. B. Tippett

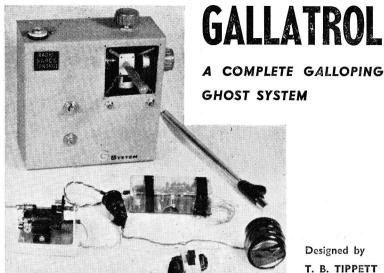

Designed by T. B. TIPPETT

WITH SEPTEMBER 1965 RADIO CONTROL MODELS & ELECTRONICS

THE basic system used is "Simpl Simul" or "Galloping Ghost", offering simultaneous proportional control of rudder and elevator with trim on each—suitable for 25 in. to 56 in. wing span models. With the larger size use of balanced surfaces is advised.


Transmitter

The transmitter is controlled by a specially developed pulser. Output is variable mark space of 80/20, 20/80 and variable pulse rate of 2 c.p.s. to 12 c.p.s. The space is filled with carrier and mark is for interrupted carrier wave tone. The complete circuit is built on a 6 in. x 3 in. p.c. board and uses 10 transistors. No relays are used. Batteries, circuit and control stick assembly are housed in a 6 in. sq. by 2\s in. deep aluminium case with a collapsible centre loaded aerial. 13.5 volt supply is used; 3 x 4.5v. and current drain is 70 mA.

Description of Tx Circuit

A conventional crystal controlled oscillator generator R.F. (VT1) and this is amplified by (VT2) in grounded base configuration, the centre loaded aerial forming the turned circuit. Current consumption of the amplifier is approximately 45 mA.

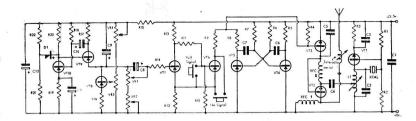An NPN switching transistor is connected in the supply to the R.F. amp, and is complementary coupled to two outputs. (1) The output from the multivibrator tone generator and (2) The output from the pulser. Both




THEORETICAL CIRCUIT OF TX AND PULSER

FIG. 1

VR2 VR3 VR4 C1 C2 C3 C4 C5 C6 C7 C8 C9		10K linear pot. 10K linear WW pot. 10K linear 01μF 33pF 01μF 01μF 05μF 05μF 105μF 105μF 105μF 105μF 105μF electrolytic 110μF + 50μF) 8μF electrolytic	VT7 : OC72 VT8 : OC72 VT9 : OC33 VT10 : OC72 D1 : OA81 Xtal : 27 Mc/s (third overtone) L1 : 15 turns, 22 s.w.g., e.c.w. on ¼ in. dia. former, tap at ¼ turns R.F.C.'s : Mac Pack type (1 Amp. T.V. choke rewound one layer 40 s.w.g., e.c.w.)
C10	:		Amp. T.V. choke re-
	:		
	:		Aerial : Teleradio tunable,
			centre loaded type
V12			Full Signal : Continuous tone
VT3			No Signal: Continuous carrier
	VR3 VR4 C1 C2 C3 C4 C5 C6 C7 C8 C9	VR3 : VR4 : C1 : C2 : C2 : C5 : C6 : C7 : C8 : C9 : C10 : C11 : C12 : VT1 : VT2 :	VR3 : 10K linear WW pot. VR4 : 10K linear C1 : .01 μF C2 : 33 pF C3 : .01 μF C4 : .01 μF C5 : .01 μF C6 : .05 μF C7 : .05 μF C8 : 2μF electrolytic C9 : 150 μF electrolytic (100 μF + 50 μF) C10 : 8μF electrolytic C11 : 100 μF electrolytic C12 : 100 μF electrolytic VT1 : 2N708 VT2 : 2N697 (with heat sink)

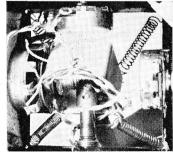Heading photo shows the neat appearance of the Tx, compact Rx and simple Servo, Below: Pot linkage in Tx, Rx right.





Tx Assembly

Component No.	Over and in hole No.	To hole No.				
	R	ESISTORS			REMARKS	
1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22	2 13 17 37 71 53 68 50 40 79 105 101 111 98 91 76 65 62 42 59	14 14 36 70 52 69 51 39 80 84 104 110 112 1118 97 77 64 61 35	3.3K 6.8K 100 2.2K 47 4.7K 4.7K 3.9K 22 10K 1K 47 47 100Ω 330Ω 23Ω 33K 1L 1.5K 3.3K	Orange Blue Brown Red Yellow Orange Yellow Orange Red Brown Brown Yellow Yellow Orange Red Brown Orange Brown Orange Brown Orange Brown Orange Brown Orange	Orange Grey Black Red Violet Violet Orange Violet White Red Black Violet Violet Violet Grange Red Orange Red Orange Red Orange Red Orange Red Orange	Red Red Brown Red Red Orange Orange Red Orange Red Orange Red Red Orange Red Red Orange Red Red Orange Brown Black Orange Red Red Red Red Red Red Red

		CAPACITORS	RFC1 RFC2	24— 25—		Macpac type Macpac type				
-1	5— 6	.01	Diode	46	43 C	A81 -	⊢ VE to 46			
2	21—22	33pF	Xtal	11—	3 2	/ M/c	3rd overtone			
3	9-10	.01		E	В	C	TYPE			
4	18-19	.01	VTI	8	4	7	2N708			
5	27-28	.01	VT2	32	31	30	2N697			
6	72—54	.05µF	VT3	34	38	33	OC139			
7	67-49	.05µF	VT4	74	66	73	OC83			
8	115-114	$2\mu F$ + VE to 114	VT5	56	55	48	OC83			
		I VE	VT6	83	86	82	OC72			
9	93—94	$150\mu F + (100\mu F + 50\mu F) = 94$	VT7	103	110	102	OC72			
10	75-78	$8\mu F$ + VE to 75	VT8	106	107	108	OC72			
11	41—47	$100\mu F + VE \text{ to } 41$	VT9	95	88	90	OC83			
12	45-44	100 #F + VE to 44	VT10	57	63	58	OC72			

Wiring


4

18 in. length in each hole light flexible.

NOTE: Bind to pot lugs to prevent fracture.

Hole		
No.	Colour	To
121	Red	+ VE 12v. or 13.5v. Bat. via switch
117	Black	Rate trim pot wiper (RV4)
88	Red	Rate pot one side (RV3)
109	Yellow	Wiper rate pot (RV3)
96	Red	M/S trim pot wiper (RV2)
113	Green	M/S pot wiper (RV1)
116	White	M/S pot wiper one end (RV1)
99	Blue	One tag on each of FS and NS buttons
87	Orange	Other tag on FS button
81	Brown	Other tag on NS button
120	Black	—VE 12—13.5v. Battery
Furthe	r Connect	
Free e	nd RV1 to	one end RV2
Free e	nd RV3 to	one end RV4

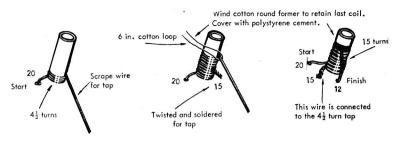TX FULL SIZE **PLACEMENT** R2 C_3 DIAGRAM FIG. 2 23 Hold up to the light to identify 0 20 G aliminium screen 1½" high p.c. lands. C12 R8 R22 R20 R R5 R18 R17 <u>R</u> 9 R14 82




TX COIL WINDING SHOWN IN THREE STAGES

FIG. 4


TX COMPONENT PLACEMENT

FIG. 5

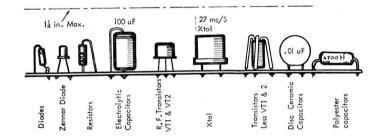

pulser and tone generator run continuously. Consider for a moment the output from the pulser to be in the 'off' condition (i.e., VT6 off. The base of VT3 will then see the tone generator wave form across R4, the transistor will respond to this and switch the R.F. at tone frequency. Now consider the pulser output to be 'on' (VT6 on), VT3 will now see a min. voltage level across R4 caused by the divider R9-R4; this is sufficient to keep it fully on during the 'off' periods of the tone generator. It follows then that when the pulser output is on, carrier is transmitted and when the pulser is off tone is transmitted.

A Schmitt Trigger forms the output of the pulser ensuring clean switching. The Schmitt is connected to a sawtooth wave form generator who's frequency is variable forming elevator control. The point at which the Schmitt triggers on the sawtooth is variable forming variable M/S or rudder control. These two variables are connected to a single joystick giving two independent proportional channels with 'in series' pots wired in to give in flight trim. With component values shown the Tx output is suitable for Galloping Ghost.

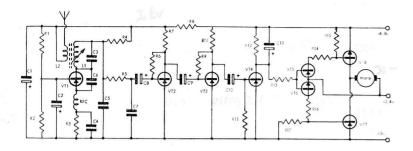

THEORETICAL CIRCUIT OF RX & SERVO AMPLIFIER

FIG. 6


REC	IVE	R VALUES	R14 R15	di	150Ω 1K	VT1 : VT2 :	OC170 OC44
R1 R2 R3 R4 R5 R6 R7 R8 R9 R10		4.7K 2.2K 4.7K 4.7K 6.8K 220K 4.7K 1K 470K 4.7K	R16 R17 C1 C2 C3 C4 C5 C6 C7 C8 C9		150Ω 1K 50/80 μ F electrolytic 2 μ F electrolytic 22pF .001 μ F .005 μ F .25pF .32 μ F electrolytic .32 μ F electrolytic	VT3 : VT4 : VT5 : VT6 : VT7 : VT8 : L1 :	OC44 OC42 or OC72 2N1305 2N1304 2N1305 2N1304 8½ turns 24 s.w.g. on ¼ in. dia. former 3¼ turns thin p.v.c. wire wound over L1 Mac Pack type
R12 R13	:	2.2K 1K	C10	i	$1 \mu F$ electrolytic $3.2 \mu F$ electrolytic	Aerial :	

Receiver


Doug Bolton's "Flexitone" (modified) built on 3 in. x 1\mathbb{s} in. p.c. board with "push pull" output. A total of 8 transistors are used.

FIG. 7



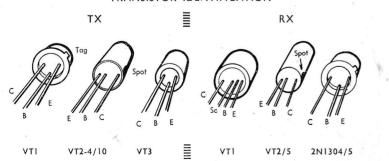

TO REMOVE LIFT TOP STAPLE

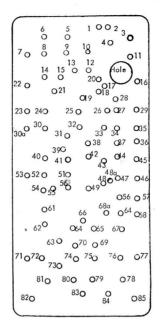

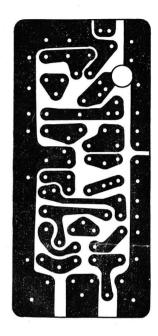


FIG. 8


RX P.C. BOARD FULL SIZE HOLE IDENTIFICATION

FIG. 9

FIG. 10


COMPONENT PLACEMENT ON RX


L1 & L2 COIL WINDNG DETAIL

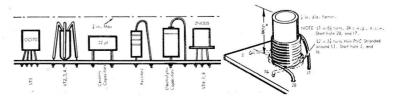

Rx Assembly


	RI	ESISTORS				RE	MARK	S				
Component No. 123 4 5 6 7 8 9 11 123 14 5 16 17	29	C4/RFC 27 C8/C7 33 34 48 48 47 52 64 57 67 70	4.7K 2.2K 4.7K 4.7K 6.8K 220K 4.7K 1.K 470K 4.7K 4.7K 2.2K 1. 1.50Ω 1.K 1.50Ω 1.K	Yellow Red Yellow Yellow Blue Red Yellow Yellow Yellow Red Brown Brown Brown Brown Brown		Re Vic Gre Re Vic Bla Vic Vic	olet olet olet ck olet olet olet olet olet olet olet olet		F F F F F F F F F F F F F F F F F F F	Red Red Red Red Red Red Red Red Red Red	ow ow :k	
		CAPACIT	OPS				YD	NICIC	TORS			
1 3	4		OμF + VE	to 4		Е	C	414313 B	SC			
2 5	— 9 —26	2μF 22pF	+ VE to 5	*Arvich	VTI	15	20	13	12		OC17	70
4 7	-RFC	/R3 .001			VT2	39	38	31			OC44	
5 23	—24 3—21	.005			VT3	41	49	42			OC44	1
	A—R5	25pF C8 .05			VT4	40	55	51			OC72	2
8 30	R5,C	$.32\mu$	F + VE to 3	0	VT5	66	67	60			2N13	05
	44 49		+ VE to 50	Terres (A	VT6	64	62	63			2N13	04
11 57	— 56	3.2u			VT7	81	80	73			2N13	
RFC I	4 R3	,C5			VT8	79	78	84			2N13	04
		W WY• •			Hole No.	Cole	our	c	То			
	8 in.	Wiri) length in			82 85 83 66	Red Black Gree Whit	n	Pin Pin Pin Pin	No. No. No. No.	7 1 5 3	B7G B7G B7G B7G	plug plug plug plug
					Aerial	*30 i	n. len	gth w	rire to	h	ole N	o. 1

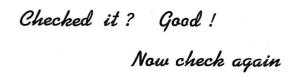

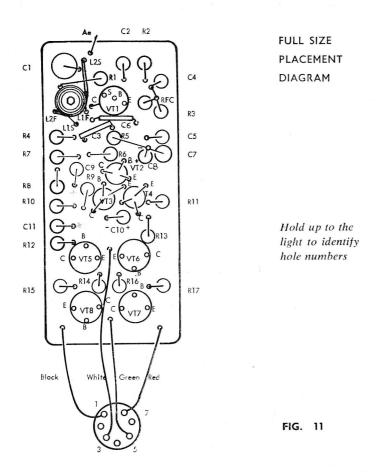

Have a care . . .

Check at every stage . . .

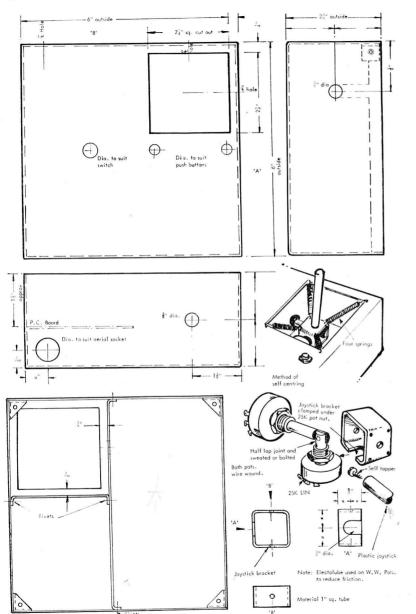

Servos

As long as "Mighty Midget" motors remain available, these are easily modified with a torsion centring spring. Battery supply for Rx and servo is 4.8v, centre tapped 500 DEAC or 225 DEAC for light weight.

Servo Coupling

Fig. 3 shows a typical servo to control surfaces link-up. The success of the system depends upon correct linkage to give the required throws of elevator and rudder.

(1) It is easier to get the required throws of surfaces if rudder and elevator hinges and *end* of brass crank bearing are kept in the same vertical line (see sketch).


(2) A good idea is to finish model completely, servo installed, torque rod, etc., but the tail block with the brass bearing in is deliberately cut small and left unstuck, i.e., free to move up, down, left, right.

Now careful bending of crank and cutting of block to move the pivot point will easily lead to the correct alignment and surface throw when satisfied wedge and stick well with cement. This saves bending the wire loops and crank to the most odd shapes to attain correct operation. Before leaving the subject of servo linkage it must be mentioned that the movement of the servo and linkage must be as friction free as possible.

Due to the limited power available from the servo the size of model is limited to about 56 in. span and on the larger size of model balanced surfaces can be used with advantage.

FIG. 12

DETAILS OF TX CASE AND POT LINKAGE

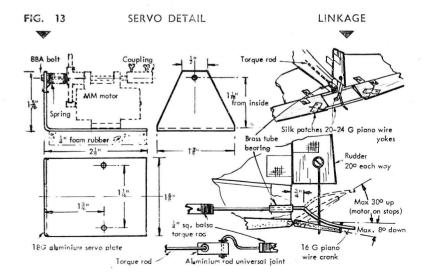

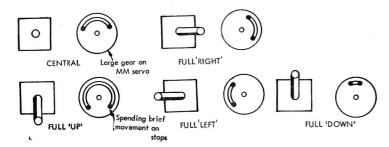


FIG. 14

COMPLETE SYSTEM CHECK

Testing Tx

- 1. Make sure all components are in correct position.
- Set trim pots to half way position.

Set L1 core into coil.

Set extended aerial.

Set up meter in -VE line on 100 mA scale.

- Connect supply leads to a 9-13.5v. supply.
- Switch on for a brief moment just long enough to ensure that the current drain is approximately -70 mA if there is much more current drain disconnect and check over again. If current is correct or less carry on with test.
- Check with R.F. meter that there is some R.F. present at the aerialslowly turn out core of L1 noting the corresponding rise in R.F. to a maximum where further unscrewing will produce a rapid fall in R.F. -turn back until R.F. suddenly appears then turn in one complete turn.
- To tune the amplifier adjust aerial coil slug in or out to obtain maximum R.F. strength.

The tuning of the aerial coil produces a fairly rapid but smooth

fall off in R.F. either side of the correct tuning point.

Final tuning should be carried out with p.c. board installed and one hand on Tx case.

7. The note from the Tx (if any) should now be studied, a crystal earpiece with one end of the jack plug held on the aerial or better still connected to the R.F. meter is required.

Adjust the main pots (M/S and Rate) to provide pulsing—the M/S pot first to "find" the pulses. (Too much to one side will be full tone and too much to the other side, just carrier.) Once the pulses are "found" adjust the rate pot to give about 2½-3 c.p.s. with the stick in fully down position. Set the M/S pot so that pulsing still occurs at both extreme right and left movement of the stick.

The Tx is now roughly set up. Final R.F. tuning and pulser setting should be done in conjunction with the Rx. Servo response to stick movement is shown in Fig. 14. Don't worry about "in-between" movements they will sort themselves out providing the right, left, up, down, are O.K.

Rx Testing

- Check component positioning.
- Connect batteries and servo.
- Switch on for a brief moment—servo should drive to one side stop after 'flipping' to the other one first.
- Check with R.F. meter that R.F. is being transmitted from the Rx aerial (only weak signal), this shows that front end is working.
- Switch on Tx and tune L1 (Rx) in or out to receive the pulsed signal.
- Proceed to line up equipment as previously explained.

System Specification

All transistor Tx. Weight: 21 lb. plus batteries

Size: 6 in. \times 6 in. \times 25 in.

Room for 12v. (2 x 6v.) DEACs approximately $5\frac{1}{2}$ hours capacity.

All transistorised Rx. Weight: 24 oz. including plastic case push/pull output, no relays.

Supply: 4.8v. servo battery.

Servo: Modified M.M. motor. Weight: 2½ oz.

All up flying weight: 225 DEACs = 7 oz. 1½ hours capacity. All up flying weight: 500 DEACs = 9 oz. 4 hours capacity.

Combined range = 500 yards.

Notes

Do not let Tx supply go below 9v. or pulsing will stop (Zenner diode stops switching at 8.2v.).

Do not leave Tx switched on for lengthy periods with no aerial load. Output transistor gets hot. (The 15 ohm emitter resistor should prevent any damage in any case.)

Complete set of components and mechanical parts or completely assembled outfit is available from the designer.

Suitable models



Try something from the M.A.P. Plans Service . . . 'Rattler", RC734 8/6d., was designed for Galloping Ghost



VERYONE who starts making models of any kind soon gets to hear of AĔROMODELLEŔ & MODEL MAKER PLANS SERVICE and the magnificent full-size working drawings that it offers. The selection numbers over a thousand differ of model designs, including boats, racing yachts, cars (vintage, veteran, modern and racing), power boats, naval craft, submarines, schooners, marine miniatures, aircraft, gliders, flying boats and workshop accessories-in fact, a fantastic list, which is justly claimed as the widest and finest in the world. Such a list deserves a fine catalogue, and the PLANS HANDBOOK comprises no fewer than 160 pages, $7\frac{1}{4}$ in. by $4\frac{3}{4}$ in., with nearly every drawing on offer duly illustrated. In addition, it was found that so many would-be builders had similar queries that now it is more than a catalogue; it is also a text-book in miniature to set newcomers on the right road from the start. In over sixty countries half-a-million copies of previous editions of this Handbook Catalogue have been sold. YOUR COPY is waiting at Model Aeronautical Press Ltd., 30-35 Bridge St., Hemel Hempstead, Herts, and will be sent immediately on receipt of your postal order for 2s. Articles by experts cover the most usual sources of difficulty and deal with such subjects as:

BUILD!NG FROM PLANS: SCALING PLANS UP OR DOWN: STARTING & OPERATING DIESEL & OPERATING TRIMMING TOWN PLUG ENGINES: DOPING: TRIMMING FOR FLIGHT: RADIO CONTROL FOR AIRCRAFT: F.A.I. REQUIREMENTS: PLASTIC MOULDING: DATA ON THE WORLD'S MODEL I.C. ENGINES: COVERING WITH SILK: and a host of other useful items of information.

Latest fully illustrated catalogue and handbook featuring over 1,000 plans. Group headings include the following main divisions : FLYING SCALE AIRCRAFT in every category : FREE FLIGHT POWER : CON-TEST POWER: A2, OPEN-CLASS & A/1 GLIDERS: RUBBER MODELS: WATERPLANES : INDOOR WATERPLANES: INDOOR
MODELS: RADIO CONTROL: CONTROL LINE
SPORT, SPEED, STUNT,
TEAM RACING: SOLID
SCALE PLANS: RACING YACHTS: SAILING CRAFT: POWER BOATS: AIR-SCREW DRIVEN HYDRO-PLANES : STEAM ENGINES CARS including TOTYPE PLANS : HOVER-CRAFT : MARINE MIN-IATURES : BOOKS FOR MODELLERS.

(C)

Copyright: MODEL AERONAUTICAL PRESS LTD.,

30-35 Bridge Street, Hemel Hempstead, Herts.

Printed by: BLETCHLEY PRINTERS LTD., Central Gardens, Bletchley, Bucks.