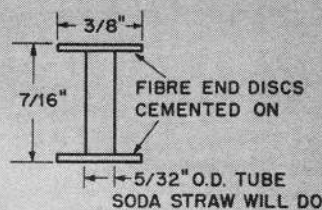


2 "C" PIECES EACH SIDE, MADE AS IN ORIGINAL ARTICLE. BEND DOWN AFTER ASSEMBLY

L3 WINDING FORM



CK5854, as noted in the Parts List and elsewhere in the text.

"High Speed Circuit." The receiver was used all year in a proportional plane with rudder-only, operated at moderately high pulse rate, and gave fine results. It was also found amply fast enough to "catch" the second and third positions of compound escapements. However, when a dual-proportional system utilizing pulse-rate change for the elevator was installed, we found as expected that the set lost out at higher pulse rates. A rehash of the circuit plus a new trans-

Our famous Tech-Two radio control receiver has been converted to 27 $\frac{1}{4}$ and 220 mc! Howard McEntee says . . .

Everyone's in on the Act!

■ Talk about response! From all over have come queries, suggestions and comments on the 50 mc Tech-Two receiver which appeared in the 1957 *A.T. Model Annual*. With many new adaptations of the circuit by readers, it's a good time for a roundup of info on this very satisfactory receiver.

The radio control receiver shown in the original article was flown in many parts of the country. The set is by far the simplest and most reliable CW receiver (meaning that it is used with unmodulated transmitters) we have used yet. Let's look at ways to make it even better—and more versatile.

27.255 Mc Operation. As noted in the *Annual* article, 27 $\frac{1}{4}$ operation had not been perfected at the time the 50-mc receiver was put in operation. It was soon found this was easily accomplished; in fact, the "secret" was inserted in the circuit of the 50-mc set just before the article went to the printer (since it makes this one work better, too). It is simply C4, and for the circuit given on page 50 of the *Annual*, C4 should be about 150 mmf. L1 should be 32 turns of #30 en. wire on a CTC type LSM form, with red core. L2 should be 3 turns of thin insulated hookup wire wrapped around the center of L1. Grid leak R1 should be dropped to about 1.2 meg. The interstage transformer and all other components are just as shown in the *Annual*. With this setup we got idling current of .35 ma for V1, and no-signal plate current of V2 was about 0.6 ma. With a fairly strong signal, V1 drops to .33 ma, and V2 rises to 2 ma or a bit higher.

It's interesting to note that this receiver is very tolerant to changes in



relay resistance, in fact you can use relays from 5,000 to 10,000 ohms, with little difference in idling and on-signal current. This being the case, it's smart to use a high resistance, since—within reasonable limits—the higher the resistance you use the more "sensitive" the relay; in other words, you will be able to apply more spring tension for a given operate-and-release current. This, a big help where engine vibration is troublesome, is just general good practice anyhow.

Article Corrections. Sad to say, a couple of errors appeared in the original article. A ground connection should be made to the filament of V2, right side of C3, and bottom of R3 and the diode. This would probably be obvious to most builders, since the filament wiring is usually put in first. Another correction: in the caption, center of page 50, V2 is referred to as a "CK5857." It is really a

former (L3 and L4) took care of this; the "fast" circuit will follow pulses reliably up to about 12 per second. In fact, we feel the limiting factor is now the relay, and not the receiver circuit itself.

The new circuit shown atop pages 28 & 29 is the 50 mc version. All the lag came from the components around V2, but when these were changed it was found necessary to get considerably more step-up in L3-L4, to retain the same V2 idling current that we had with the original receiver. This meant many more turns in L4, and fortunately it turned out that a 5,000 ohm Gem relay coil was just the ticket. This enabled us to reduce the size of the transformer; details are given. The same core material as in the original was again employed, but note that there are only two "C" pieces inserted into each side; no "I" strips are needed. Balsa strips, cut to fit into the coils and jam the core pieces,

220 Mc Tech-Two By Pete BLISS

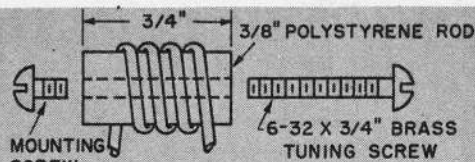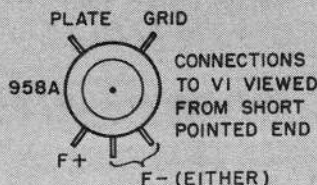

- L1 - 4 TURNS #16 WIRE SPACED ONE DIA. BETWEEN TURNS, CENTER TAPPED
- L2 - 1/2 TURN INSULATED WIRE AT PLATE END OF L1
- RFC - 30 TURNS #30 E 1/8" DIA., CLOSE WOUND AND SELF SUPPORTING APPROXIMATELY 1 UH



DWG. 4

7 1/16"

1/4" TUBES

5/8"

L3
2000
TURNS
#42 EN

L4
7500
TURNS
#42 EN

2 "C" STRIPS IN EACH
SIDE. ADD 2 "I" STRIPS
IN L3 AND 14 IN L4.
BEND "C"'S FLAT AFTER
ASSEMBLY

9 1/16"

the Wipmac is always complete) down to the cement. Jolly well smashed. All this only 100 yards from the transmitters. Harold deBolt pls note: Cruiser's only damage was cracked wing tip.

Contest Calendar. Fourth King Orange "Internationals" at Miami, Fla, December 27 through 30. Control, free flight, glider and radio events. Great gathering, go if you can. Write C.R. Quick, 1896 N.W. 36th St., Miami, for info.

Second annual Ravin' Cajuns' control line meets at New Orleans, La., on December 28 & 29. Director is P. A. Burvant, 77 Spanish Fort Blvd.

Indoor air meet for gliders, pre-fabs, paper and microfilm covered endurance models at Cleveland's Public Hall on January 5. Also, the 11th annual National Scale Model Plane Show (no flying, just static exhibits) is scheduled for March 28 through 31 at the Higbee auditorium. Categories and age divisions to appeal to all scale assemblers and/or flyers. For data on either event write Charles Tracy, "The Cleveland Press," Cleveland, Ohio.

Thirty Per Day. "We have been receiving applications from your readers at the rate of 20 to 30 per day but we regret to say that only in 2 cases have they had the courtesy to send any payment or postage and for quite a lot we just cannot decipher the writing." This is the Precision Model Engineering Company of 49 Whitechapel, Liverpool 1, England, writing. Seems like they were flooded by inquiries after our article of last October, "Sports Car Racing in Your Living Room" which concerned electric powered model cars.

Guess we should have suggested that when writing Precision (makers of the cars, gears, motors and allied d.c. race accessories) you enclose something to cover data sheets and mailing costs. Outfit now has a new 12-page "Electric Rail Car Racing Manual" and although they don't specify what their idea of "proper remittance" to be we suggest you send an international postage coupon of 50c value (you get it at the post office). Above all, print your name and address. If you wrote Precision and haven't heard from them (they sent out a descriptive sheet and letter) it means they couldn't read your writing. Drop 'em another note, typing or printing your return address and enclosing the 50c coupon.

Hail, Tacoma! Clover Park High School is teaching model building to a class of 10 specially selected students. Van Lehman says it is the only class of its kind in the Northwest. He's taking the opportunity to learn how to make good scale planes.

Everyone's

(Continued from page 21)

length including the wire from the end of L2 to the bottom of the antenna should be about 2 feet. Actual antenna coupling is varied by using more or less turns on L2 or by moving L2 away from the center of L1. To check if you have too much antenna loading, put your finger on the antenna; plate current of V1 should rise a bit, and that of V2 should drop a little. If both rise to a high value, you have too much antenna loading; either reduce the antenna length or reduce turns in L2. This is not actually mandatory, as the set will work well with too much coupling, but you might as well have it adjusted right. There is no need to use a variable condenser in the antenna lead as is often necessary with single hard tube receivers.

8. Lowest idling current of V2 will come at a rather low value of V1 grid leak (R1), but the set should not be operated this way, as it will be more sensitive to dropping battery voltages; it will also not be as sensitive to weak signals. Better not change R1, unless you decide it is necessary, after checking Step 3.

ADDITIONAL HINTS. Although not shown on the original Tech-Two circuit, it is smart to use an electrolytic condenser of about 1 mf and 50 volt rating for B plus to ground; this makes it necessary to break both the A and B leads to the set, since the electrolytic will have a slight leakage current, even when the set is off. The original Tech-Two has never had this condenser, and it is really not needed, providing you always use good B batteries and don't let them drop too low. The 27½ and 50 mc receivers will work on as little as 38 volts (with reduced relay current), but a B battery that drops this much is sure to have high internal resistance, which will render the receiver inoperative unless the electrolytic is used. Modern sub-miniature condensers of 5 mf capacity and 50 volt rating are only about ¼ x ¾" in size.

Some commercial RF chokes have been found to work fine in the Tech-Two. The Miller #6152 Video Peaking Coil (which is equivalent to a 20 microhenry RF choke) works well in both the 27½ and 50 mc circuits. For these two frequencies, Gyro 22 mh and 10 mh iron-core RF chokes have been found ideal and are extremely small.

If you require more plate current change than can be had from the CK5854, the old reliable 1AG4 will do fine provided you install a screen grid resistor and condenser, as shown in Dwg. 5. Don't use this tube without the resistor, as the current will go to a high value and "stick" there till you open the B circuit. The 1AG4 will give the same results in both 27½ and 50 mc sets, of course, with signal-on current in either case of about 3.3 ma. Idling plate current will run about .7 ma. Note that screen grid current of any tube used as V2 will be about .1 ma with no signal, and from .6 to .9 ma with signal; after you have checked plate currents of both tubes as noted in this article, you can thereafter use just a single meter in the B plus lead to the entire receiver. You will know that V1 changes very little with or without signal, and that around ¾ of what the meter reads is the actual "working" current of the receiver—the current that operates the sensitive relay.

This brings us pretty much up to date, though not entirely. New developments on the Tech-Two are in the works, among them replacement of the second tube with transistors. This may make necessary only 22½ volts for the entire receiver! Meanwhile try the circuits and modifications shown. Let us know how you make out.

Hothead

(Continued from page 19)

to keep them from warping from the pull of the covering. After the tip plates are glued in place, sand the whole frame and cover with silk or double-cover with paper.

Stabilizer ribs are cut to shape without notches, glued into slotted trailing edge, then the leading edge and tips glue into place. The spars are pinned over the top of the ribs using a straight edge as a guide. With a sharp razor blade, cut down into the ribs on the front and back of the spar for the correct depth. Spar is removed, the notches broken out, the spar glued into position. Don't forget the hardwood center piece on the nose of the stab. The stab should be covered with either light weight silk (about 3 momme handkerchiefs obtainable at Kresge stores) or tissue.

Top sheet of fuselage is notched to take the pylon, bottom sheet is notched in the rear to take rudder. We now set rudder at zero (no offset) and cut in small tab for trim. Works better. The top and bottom sheets are glued to one side and the bulkheads glued in place. When dry, the pylon and its side braces are glued into the fuselage, also the rudder